

Current events

Key Stage 4 Revision Programme

Pupil Name

Handbook
Designed by

Dr Stutchbury



Contents


Course Rationale	P4
Glossary of Keywords	P5
Tutorial 1	P6
Tutorial 2	P7
Tutorial 3	P13
Tutorial 4	P20
Tutorial 5	P27
Tutorial 6	P35
Tutorial 7	P36

Course rationale

Have you switched on a light in your home today? Or maybe turned on the oven or hob to help with the cooking? Or plugged in your phone / laptop that you are working on right now?

Have you thought about what is happening between you flicking a switch and the light / heat turning on? Lots of things are happening that you cannot see before the light switches on / the oven heats up / electrical device is charging.

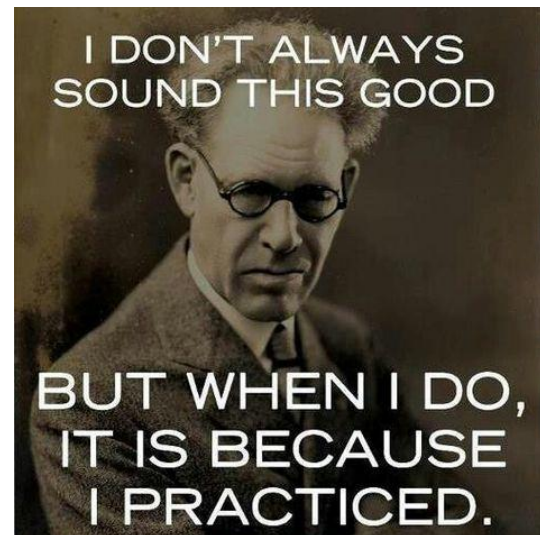This topic will help you understand how electricity works, which in turn helps you do lots of things in your life. You will be looking at currents. Understanding what currents are and how they work will help you understand how electricity works. Given that we rely on electricity A LOT, learning about currents is pretty useful to understand how so much around us works!



Why practice this topic here in the workbook?

There is a mountain of research that shows that **reading textbooks and revision guides is an extremely inefficient way to prepare for your exams**. They take a *lot* of effort for very little reward.

The best way to prepare for answering a range of GCSE questions, is to practice answering a range of GCSE-style questions. Makes sense, right?

They don't even have to be the same types of questions. The practice helps your brain understand how to answer GCSE questions. Just like practicing an acoustic guitar helps you to understand how to play an electric guitar. The skills are transferable.

And speaking of electric guitars, we need electricity to make them work. That's what we will be studying in these tutorials. Does that sound like a BRIGHT idea? ExCELLent.

WIRE we studying this, I hear you ask?

CURRENTly, this is the topic we find Year 10s and Year 11s struggle with the most in Physics. The answers are often SHOCKING. There are lots of COMPONENTS to cover - equations to remember, definitions to learn and it's really difficult to conceptualise, so you'll have to be SWITCHED ON. Some people don't have the POTENTIAL, DIFFERENCE is, you guys do.


So take this workbook, it's free, no CHARGE, and we will practice the key concepts in SERIES. I'm sure there will be some RESISTANCE and you'll find your brain HERTZ, but keeping at it is PIVitol. I'm sure you'll reach that LIGHTBULB moment. You have the POWER, so LED the way.

OHM my God, these puns are on point.

Subject vocabulary

Word	Definition
Charge	An electrical property – it can be either positive or negative. Measured in Coulombs.
Current	The rate of flow of electrical charge. Measured in Amps
Potential difference	The difference in how much energy each Coulomb of charge has at two points in a circuit. Measured in Volts.
Resistance	How difficult it is for electrical charge to flow through a component. Measured in Ohms.
Power	The amount of energy transferred by a circuit each second. Measured in Watts.
Electricity	Electricity is a type of energy that can build up in one place or flow from one place to another
Electron	The smallest of the particles that make up an atom, and they carry a negative charge
Rate	The speed at which something happens or changes

1. Switching on

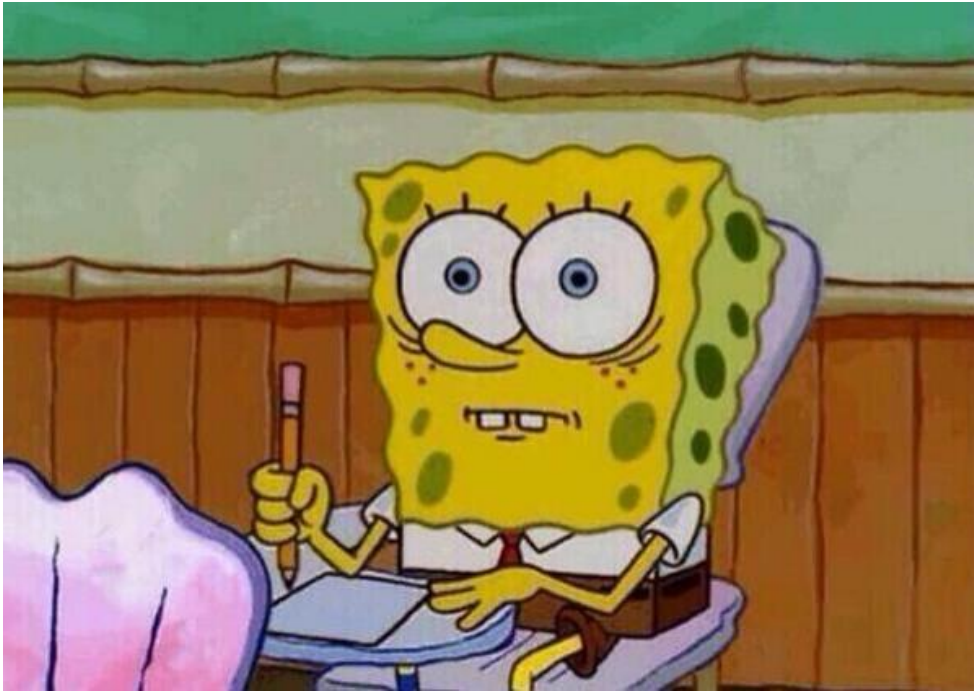

This workbook is here to help you improve your physics knowledge and understand what currents are and how they work.

2. Current events

Keywords: Current, charge, amp, coulomb, series, parallel

Objectives this tutorial:

- A) Defining current
- B) Calculating current
- C) Calculate current in series and parallel circuits


Starter: To prove that lightning is an electrical current, Benjamin Franklin allegedly flew his kite during a storm.

He attached a metal key to the kite's silk string and made sure he stood under a shelter. What was the purpose of:

The key:

The silk string:

The shelter:

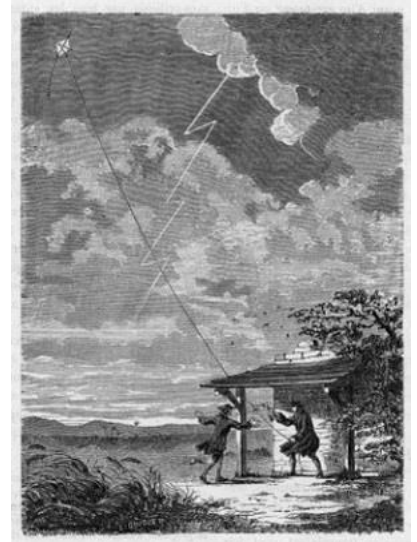

Objective A: Defining current

Charge is an electrical property – it can be either positive or negative. Current is the **rate of flow of electrical charge**. It is a rate – the amount of charge that flows through a circuit each second. In a metal wire, charge is carried by delocalised electrons.

The rate of flow of charge – the current – is defined by the equation: $I = Q/t$

- I is current (in Amps (A))
- Q is charge (in Coulombs (C))
- t is time (in Seconds (S))

If you need more help with currents check out this video here:

<https://www.khanacademy.org/science/electrical-engineering/introduction-to-ee/intro-to-ee/v/ee-current>

This means that in a current of 1 A, 1 C of charge will flow past a point in 1 second.

Note – a coulomb is a big ball of about 6.2×10^{18} electrons!

Practice A: Defining current

- 1) State the equation for current. Make sure you include the units!
- 2) From the equation, how do you know that current is the **rate** of flow of charge?
- 3) Is the charge flowing through a circuit positive or negative? How do you know?
- 4) 18 C of charge flow through a circuit in 6 seconds. Calculate the current.
- 5) (Meaty question) How many electrons flow through the same circuit each second?

Assessment A: Defining current

Which statement is incorrect?

A	1 Amp is the same as saying 1 Coulomb per second
B	If more electrons flow through a wire each second, the current will decrease
C	Ions are able to carry electrical charge through a liquid
D	Current is the rate of flow of charge

Objective B: Calculate current and charge

Worked example 1

20 C of charge flow through a circuit in 1 minute.

a) Calculate the current.

$t = 1 \text{ minute}$
 $= 60 \text{ seconds}$ ← conversion

Study tip
Don't forget to convert non-standard units into standard units!

$I = Q/t$

$I = 20 \text{ C}/60 \text{ s}$
 $I = 0.3 \text{ A}$ ← units

Study tip
To find the total number of electrons, multiply the number of coulombs by the number of electrons in one coulomb.

b) How many electrons flow in 15 seconds?

$I = Q/t$
 $0.3 \text{ A} = Q/15 \text{ s}$ ← substitute in values
 $Q = 0.3 \text{ A} \times 15 \text{ s}$ ← rearrange
 $Q = 4.5 \text{ C}$ ← units

Study tip
Only answer to the same number of decimal places or significant figures that are given in the question.

Number of electrons = $4.5 \text{ C} \times 6.2 \times 10^{18}$
Number of electrons = 2.8×10^{19}

Worked example 2

A lamp operates at 600 mA.
How long does it take for 22.8 C to flow through the lamp?

$600 \text{ mA}/1000 = 0.6 \text{ A}$

$I = Q/t$

$0.6 \text{ A} = 22.8 \text{ C}/t$ ← substitute in values
 $t = 22.8/0.6$ ← rearrange
 $t = 38 \text{ s}$ ← units

Practice B: Calculating current

1. 56700 C of charge pass through a laptop in 2.5 hours. Calculate the current of the laptop.
2. A circuit has a current of 8.5 A. How much charge flows through the circuit in 0.5 minutes?
3. A bolt of lightning transfers a charge of 15 C in 5.0×10^{-4} seconds. Calculate the current. Give your answer in standard form.
4. A student charged a power pack that could store 6 kC of charge for 6 hours using a current of 250 mA. What percentage of its capacity was the power pack charged to?
5. A set of lights consists of 20 lamps connected in series to the 50 V electricity supply. When the lights are switched on and working correctly, the current through each lamp is 0.25 A. Calculate the number of electrons passing through the circuit in 5 minutes.

Assessment B: Calculating current


Calculate the charge that flows through a thermistor in 0.2 minutes when the current is 3.5 mA.

A	0.42 C
B	4.2×10^{-2} C
C	42 C
D	0.007 C



Objective C: Calculate current in series and parallel circuits

Current is measured using an ammeter, connected in series (in line with) with the other components in a circuit. Current behaves differently in series and parallel circuits, and you need to know the difference!

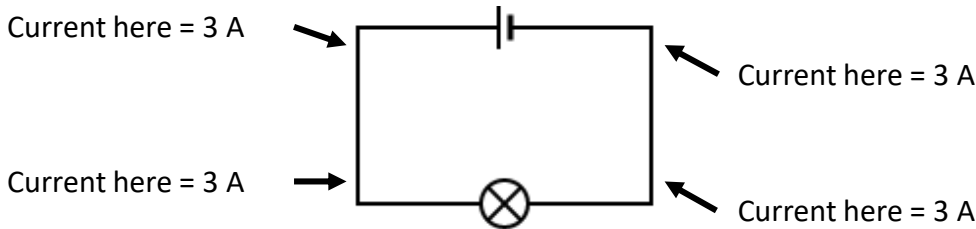In series circuits: current is the same at every point in the circuit




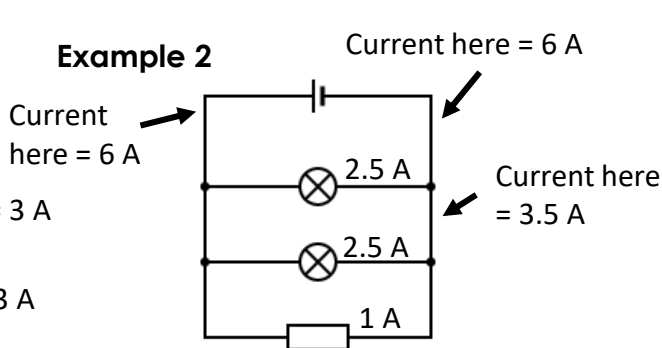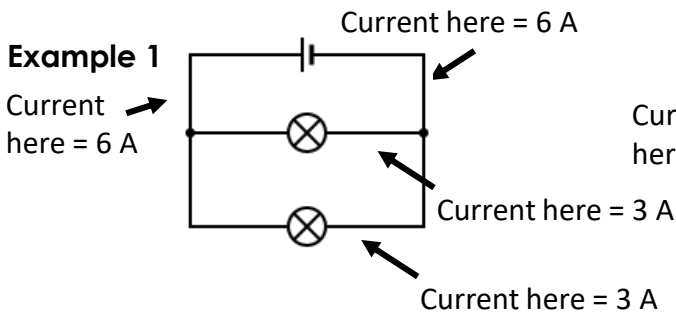In a parallel circuit: current is split between the branches of the circuit. The total current in the circuit equals the sum of all the branches. But remember, it doesn't have to split equally between them.



Worked example

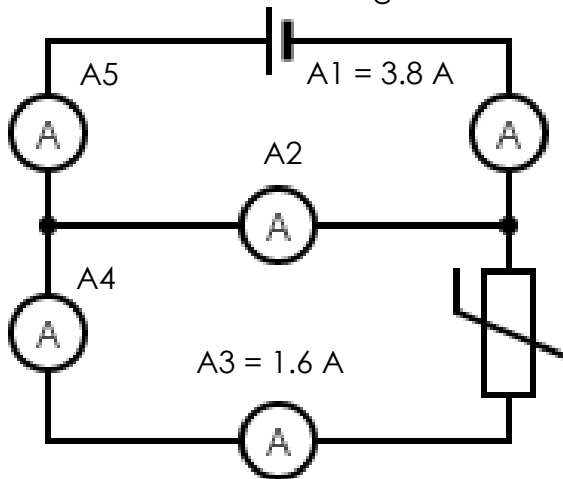Calculate the current through each of the ammeters in the circuit.



Current through ammeter A2

Before A2, the current splits between 2 loops. We know that 1.6 A goes to one branch so the rest must go to the other branch.

$$A1 = A2 + A3$$

$$A2 = A1 - A3 = 3.8 \text{ A} - 1.6 \text{ A} = 2.2 \text{ A}$$

Current through ammeter A4

This is the same loop as A3, so follows the rules for current in a series circuit:

$$A4 = A3 = 1.6 \text{ A}$$

Current through ammeter A5

The two loops come back together, so following the rules for a parallel circuit:


$$A5 = A2 + A3 = 2.2 \text{ A} + 1.6 \text{ A} = 3.8 \text{ A}$$

It is also in the same loop as A1, so behaves like a series circuit:

$$A5 = A1 = 3.8 \text{ A}$$


Study tip

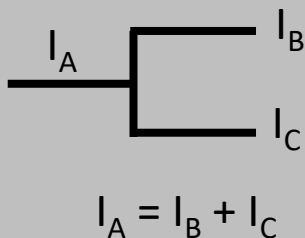Remember, at a junction, the current splits between the branches.




Practice C: Calculate current in series and parallel circuits


1. Calculate the current at each ammeter

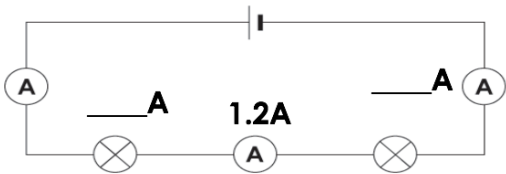

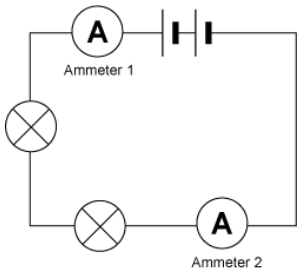
2. Dan says, “Ammeter 1 will show a lower reading than Ammeter 2 because the bulbs in the circuit use up the current.” Tom says, “Ammeter 1 will show the same reading as Ammeter 2 because current is not used up.” Who is right?



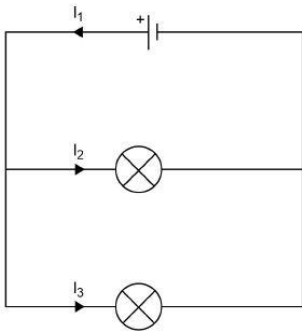3. Compare the currents I_1 , I_2 and I_3




4. Calculate the current at each ammeter

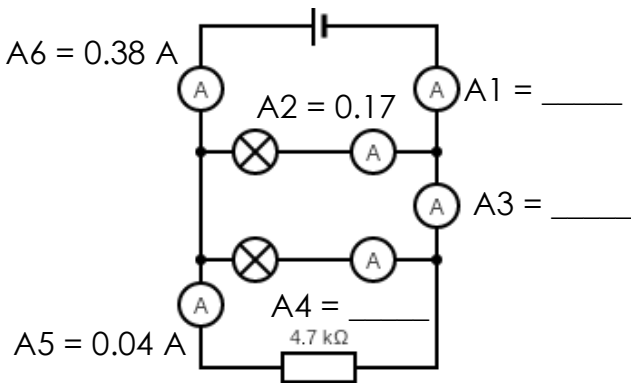

Assessment C: Calculate current in series and parallel circuits

Which equation is wrong about the following circuit?

A	$A1 = A2 + A3 + A4$
B	$A4 = A5$
C	$A7 = A1$
D	$A2 = A1 - A6$
E	$A6 = A2 + A3$

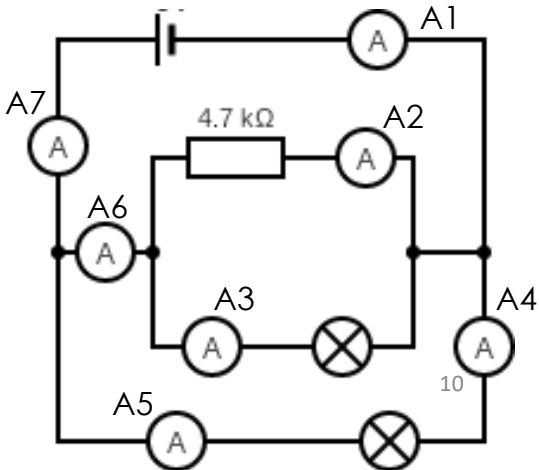

3. Potentially the same, potentially different

Keywords: potential difference, volt, series, parallel, power, watt

Objectives this tutorial:

- A) Defining potential difference
- B) Calculating potential difference in series and parallel circuits
- C) Calculating power using potential difference and current

Starter:

A delivery driver must return to the depot when they are out of packages, to get a refill.

Each time they stop, they drop off some packages, but not necessarily all of them. When they have made all of their stops, they return to the depot to collect more.

How do you think this relates to an electrical circuit?

Write down your response



Objective A: Defining potential difference

Potential difference is a weird one. It can be quite difficult to understand. It is the difference in electrical potential between two points in a circuit.

Let's break that down a bit more. It is the *difference* in how much energy each Coulomb of charge has at two points in a circuit. If at one point, each Coulomb has 7 Joules and at another point each Coulomb has 4 Joules, the potential difference is 3 Joules per Coulomb. The potential difference is 3 Volts (V).

Cells and batteries transfer energy to each coulomb of charge – they give them a push to get around the circuit. For example, a 6 V battery delivers 6 Joules of energy to every 1 Coulomb of charge.

This energy is then transferred to power the components of the circuit. The amount of energy that is transferred to a component by each Coulomb is equal to the potential difference across the component.

Note – some people say 'voltage' when they mean potential difference. This is not scientific enough, so use of the word voltage is banned.

Practice A: Defining potential difference

1) Summarise what is meant by potential difference in one sentence.

2) Potential difference is measured in Volts. What other unit could be used to measure p.d.?

3) A circuit has a 12 V battery. The potential difference across a bulb is 3 V. How many Joules does each Coulomb have left after the bulb?

4) Explain why a lamp does not light up when the batteries have gone flat

If you're still unsure what is meant by potential difference, check out this video:
<https://www.khanacademy.org/science/in-in-class10th-physics/in-in-electricity/in-in-electric-potential-potential-difference/v/intro-to-potential-difference-voltage>

Assessment A: Defining potential difference


What is the best definition for potential difference?

A	The amount of energy that is transferred between two points in a circuit
B	The amount of energy given to each Coulomb in a circuit
C	The amount of energy that is transferred by each Coulomb between two points in a circuit
D	The rate of flow of charge

Objective B: Calculate potential difference in series and parallel circuits


The potential difference across a component in a circuit is measured using a voltmeter, connected in parallel (around) the component. Potential difference does the opposite to current in series and parallel circuits, so it can, *potentially*, be confusing!

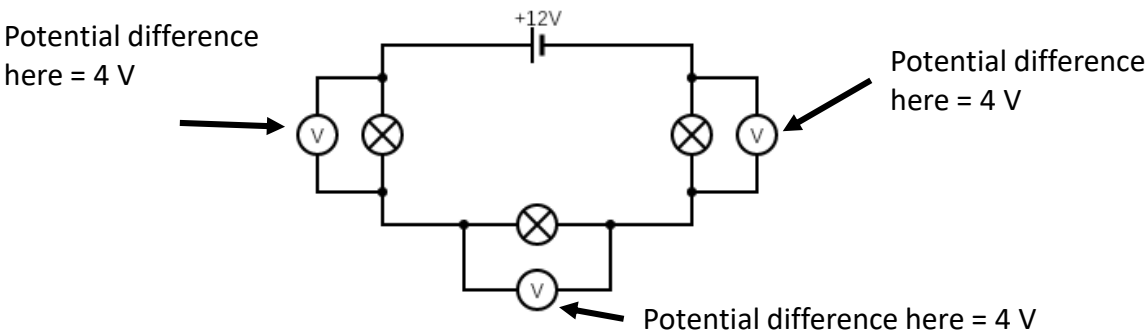In series circuits: potential difference is the split between the components in the circuit. The total potential difference provided by the power supply equals the sum of all the branches. If the components have the same resistance, the potential difference is split equally.




In parallel circuits: potential difference is the same on each branch of the circuit. If there are 2 or more components on a branch, the potential difference of that branch is shared between them.

Example 1

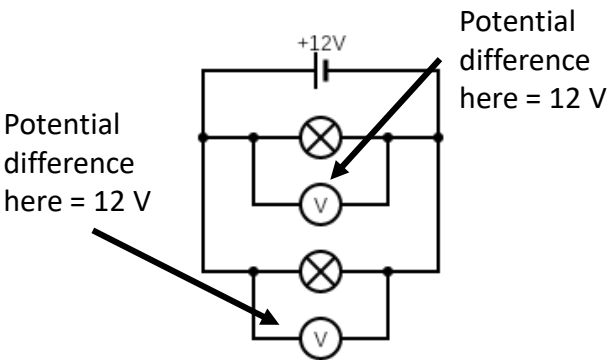


Example 2

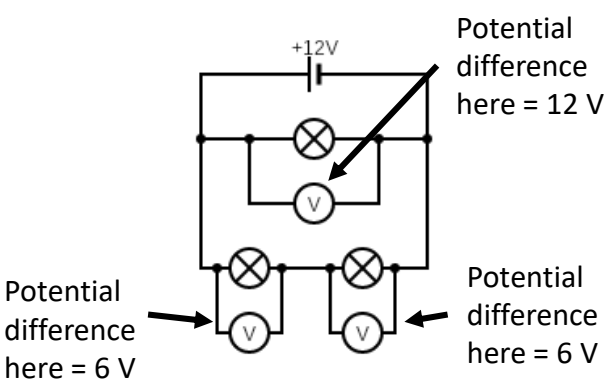

Worked example

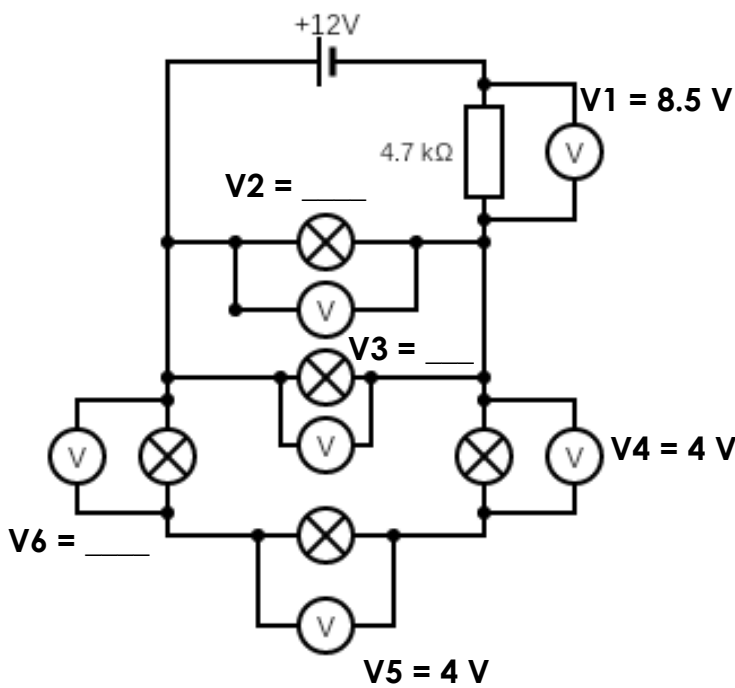Calculate the potential difference reading on each voltmeter in the circuit



Potential difference through voltmeter V2

We know that 12 V was delivered by the cell.
Before V2, 8.5 Joules per Coulomb are dropped at the resistor.

$$12 \text{ v} = V1 + V2$$
$$V2 = 12 \text{ V} - 8.5 \text{ V}$$
$$V2 = 3.5 \text{ V}$$

Potential difference through voltmeter V3

12 V are delivered to this loop and there is only one component, so all of the energy is transferred to this bulb.

$$V3 = 12 \text{ V}$$

Potential difference through voltmeter V6

12 V are delivered to this loop. Therefore, we know that:

$$12 \text{ v} = V4 + V5 + V6$$
$$V6 = 12 \text{ V} - 4 \text{ V} - 4 \text{ V}$$
$$V6 = 4 \text{ V}$$

Study tip

In series:


$$V_{\text{TOT}} = V1 + V2 + V3...$$

In parallel:


$$V_{\text{TOT}} = V_{\text{BRANCH 1}} = V_{\text{BRANCH 2}} = V_{\text{BRANCH 3}}...$$

Practice B: Calculate potential difference in series and parallel circuits

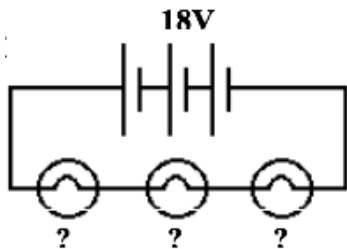1. Calculate the potential difference at each voltmeter




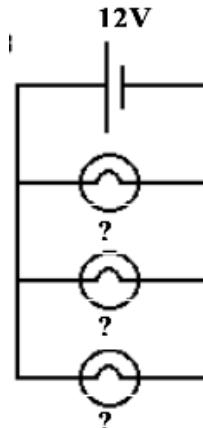2. Calculate the potential difference at each voltmeter



3. Calculate the potential difference at each voltmeter

V1 =
V2 =
V3 =

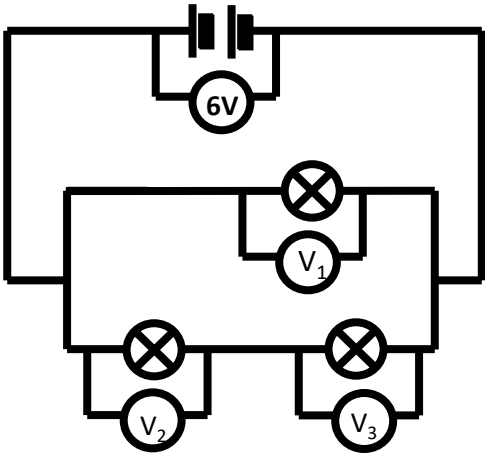

4. Which blub will be brightest in this circuit and why?

Assessment B: Calculate potential difference in series and parallel circuits

Draw circuit diagrams to show four lamps connected to a 12 V battery so that:


- a) each has a p.d of 12 V across it
- b) each has a p.d. of 6 V across it
- c) each has a p.d. of 3 V across it

Objective C: Calculating power using potential difference and current

WE KNOW SO FAR:



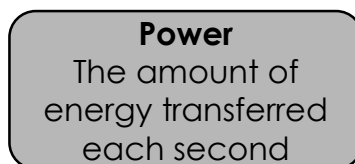
We can use these two definitions to work out **power**.



To work that out we need to know two things.

1. We need to know the amount of energy that is transferred by each Coulomb
2. We need to know the number of Coulombs that flow each second

Sound familiar?

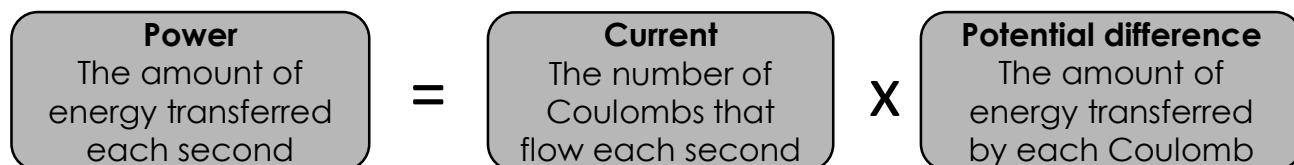

OR, put more simply

Power = Current x Potential difference

OR, even more simply

P = IV

Worked example

A new shower has a power output of 10,580 W when it is connected to the 230 V mains electricity supply.

Calculate the charge that flows through the shower in 2 minutes.

$$\begin{aligned} P &= IV \\ 10,580 &= I \times 230 && \leftarrow \text{substitute in values} \\ I &= 10,580/230 && \leftarrow \text{rearrange} \\ I &= 46 \text{ A} && \leftarrow \text{units} \end{aligned}$$

$$\begin{aligned} t &= 2 \text{ minutes} \\ &= 120 \text{ seconds} && \leftarrow \text{conversion} \end{aligned}$$

$$\begin{aligned} I &= Q/t \\ 46 &= Q/120 && \leftarrow \text{substitute in values} \\ Q &= 46 \times 120 && \leftarrow \text{rearrange} \\ Q &= 5,520 \text{ C} && \leftarrow \text{units} \end{aligned}$$

You might be wondering...

Power is measured in Watts?

No, that's it, it's measured in Watts (W).

Study tip

Don't forget to convert non-standard units into standard units!

Practice C: Calculating power using potential difference and current

- 1) What equation links power, potential difference and current?
- 2) A portable heater is connected to a 115 V battery. A current of 500 mA flows through the heater. Calculate the power of the heater.
- 3) A large machine generates 60 kW of power. How much current flows through the machine when connected to a 120 V power supply?
- 4) The charge that flows through a new shower in 5 minutes is 18,000 C.
The new electric shower has a power of 13.8 kW
- Calculate the potential difference of the power supply to the shower.

Assessment C: Calculating power using potential difference and current

The table shows the current drawn from the 230 volt mains electricity supply when different parts of the hairdryer are switched on.

	Current in amps
Fan only	1.0
Fan and heater 1	4.4
Fan and both heaters	6.5

Calculate the maximum power of the hairdryer.
Show clearly how you work out your answer and give the unit.

4. Resistance is NOT futile


Keywords: resistance, Ohm, series, parallel, current, potential difference

Objectives this tutorial:

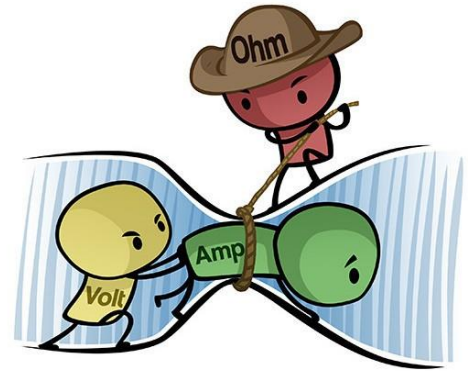- A) Defining resistance
- B) Resistance in series and parallel circuits
- C) Ohm's law in series and parallel circuits

Starter:

Using the picture, come up with a definition for resistance



Objective A: Defining resistance

Put simply, resistance tells us how difficult it is for electrical charge to flow through a component.

If a component has a high resistance, it is really difficult for the charge to get through it. If an object has a low resistance, it is dead easy for charge to flow through.

It stands to reason, therefore, that conductors have a low resistance and insulators have a high resistance.

Resistance is measured in Ohm's (Ω), named after the German physicist Georg Ohm.

Practice A: Defining resistance

1. If an object has a high resistance, what does this tell us about the flow of electrical charge through it?
2. Which object do you think has a higher resistance: a wooden pole or a piece of aluminium foil? Why?
3. Which has a higher resistance: $47 \text{ M}\Omega$ or $6.2 \times 10^6 \Omega$?
4. If the resistance is increased, what will happen to the current flowing through a component?
5. If resistance stays the same and the potential difference of the power supply is doubled, what do you think will happen to the current?

Assessment A: Calculate potential difference in series and parallel circuits

Which statement(s) are incorrect?


- | | |
|---|---|
| A | The resistance of an object tells us how hard it is for charge to pass through it |
| B | If an object has a high resistance the current passing through it is likely to be low |
| C | Increasing the potential difference has no effect on the current through a component |
| D | When resistance is constant, current and potential difference are directly proportional |

Objective B: Resistance in series and parallel circuits

Just like current and p.d., resistance behaves differently in series and parallel circuits.

In series circuits:

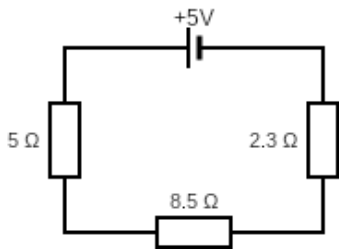The total resistance is the sum of all of the resistors in the circuit. Nice and easy.



Total resistance in the circuit =

$$5\ \Omega + 8.5\ \Omega + 2.3\ \Omega = 15.8\ \Omega$$


A simple way to write this is:

$$R_{TOT} = R_1 + R_2 + R_3...$$

In parallel circuits

This one is a little more complicated.

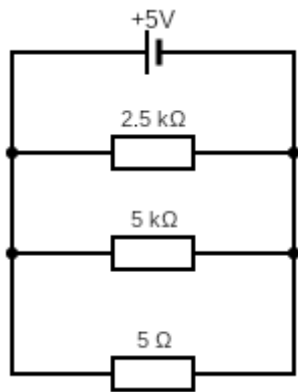The total resistance in a parallel circuit is LOWER than the smallest resistor in the circuit.



Smallest resistor in the circuit = 5 Ω


Total resistance is less than 5 Ω

You will not be asked to calculate the total resistance in parallel, you just need to be able to say that it is:


LOWER than the smallest resistor in the circuit

Practice B: Resistance in series and parallel circuits

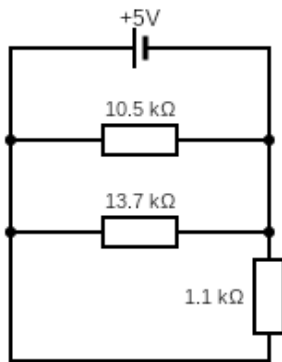
1. What do you know about the resistance of this circuit?



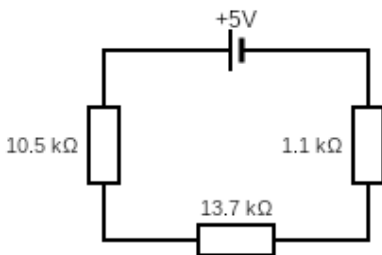
2. Calculate the total resistance of the circuit. Give your answer in Ohms, in standard form.



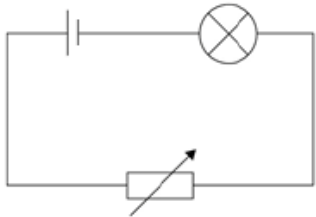
3. Another resistor is added to this circuit in series. What effect will this have on the brightness of the lamp? Explain your answer.



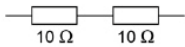
4. Which arrangement has a resistance of 10 Ω?




P

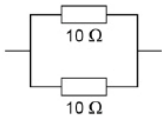

Q


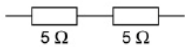


R

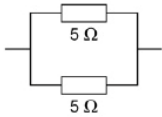

S

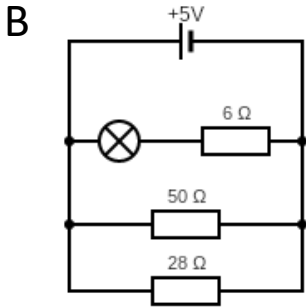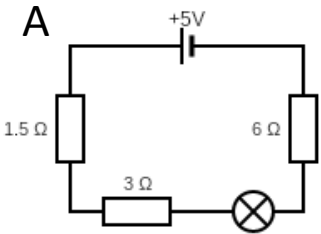
5. The circuits contain identical lamps. In which circuit will the lamp be brighter? Explain your answer.




Assessment B: Resistance in series and parallel

Calculate the resistance of each circuit

A

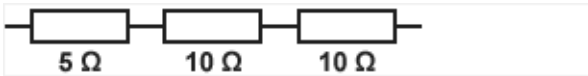

B

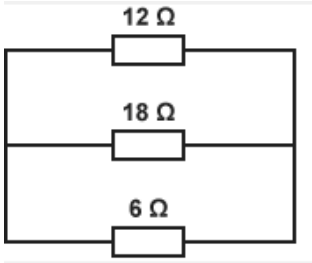

Objective C: Calculating using Ohm's law

If resistance remains constant, current and potential difference are directly proportional.

That means, if the potential difference doubles, the current also doubles.

This is called Ohm's law and can be written as the equation:

Potential difference = Current x Resistance

OR



$$\underline{V = IR}$$

Worked example 1

Calculate the reading on the ammeter. Give your answer to 2 significant figures.

$$\begin{aligned} V &= IR \\ 5 &= I \times 12 && \leftarrow \text{substitute in values} \\ I &= 5/12 && \leftarrow \text{rearrange} \end{aligned}$$
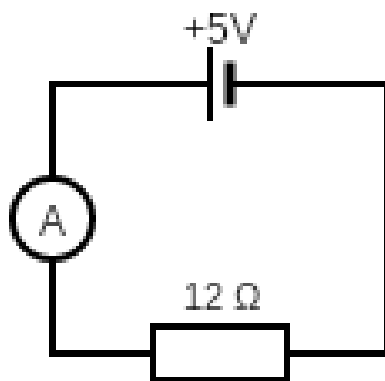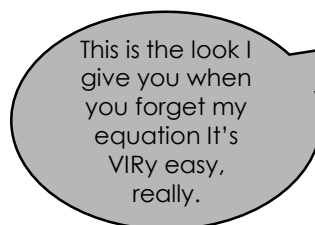
$$\begin{aligned} I &= 0.4166666..... \\ I &= 0.42 \text{ A (2.s.f.)} && \leftarrow \text{units and rounding} \end{aligned}$$



Study tip

Don't forget to give your answer the correct number of significant figures or decimal places

Worked example 2

Calculate the readings on: V1, V2, A1, A2 and the resistance of R1.

Ammeters

It is a series circuit, so the current is the same everywhere in the circuit.

$$A1 = A2 = A3$$

$$A1 = 3 \text{ A}$$

$$A2 = 3 \text{ A}$$

Resistor R1

$$V = IR$$

$$3 = 3 \times R$$

$$R = 3/3$$

$$R = 1 \Omega$$

Voltmeters

$$V1$$

$$V = IR$$

$$V = 3 \times 2$$

$$V = 6 \text{ V}$$


$$V2$$

It is a series circuit, so potential difference is shared between the components.

$$V2 = V1 + V3$$

$$V2 = 6 + 3$$

$$V2 = 9 \text{ V}$$

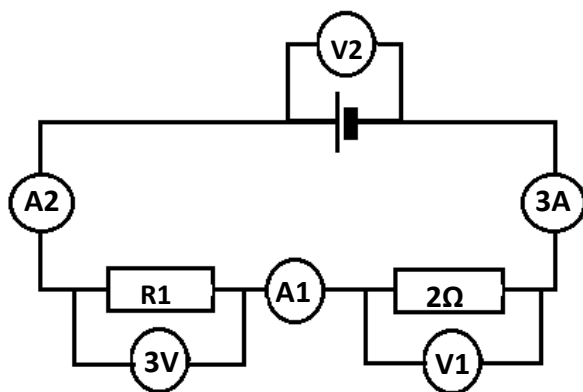


Study tip

You might be asked questions that require you to use your knowledge of circuits AND Ohm's law together.


Practice C: Calculating using Ohm's law

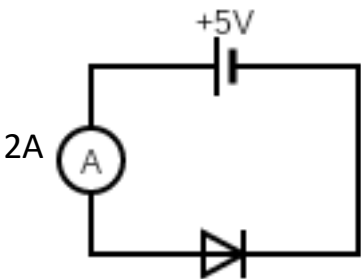- 1. What is Ohm's law?
- 2. The potential difference of a circuit is halved. What happens to the current? Why?
- 3. Calculate the resistance of the diode. Give your answer to 3 significant figures.




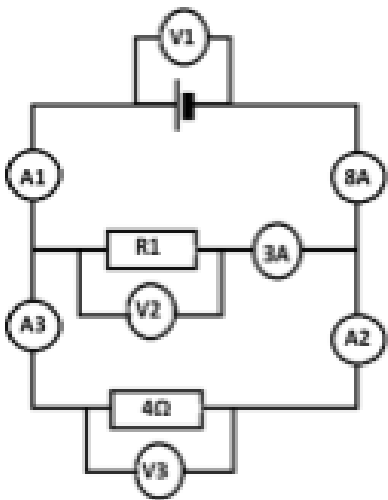- 4. Calculate the values at each point specified

A1 = _____
A2 = _____
A3 = _____
V1 = _____
V2 = _____
V3 = _____
R1 = _____




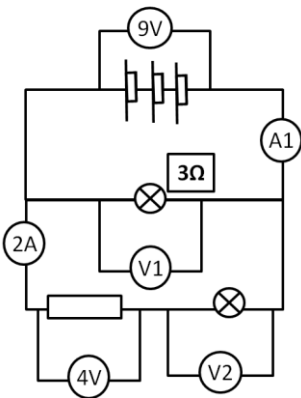- 5. Calculate the values at each point specified.



A1 = _____
V1 = _____
V2 = _____
Calculate the resistance of:
The bulb = _____
The resistor = _____

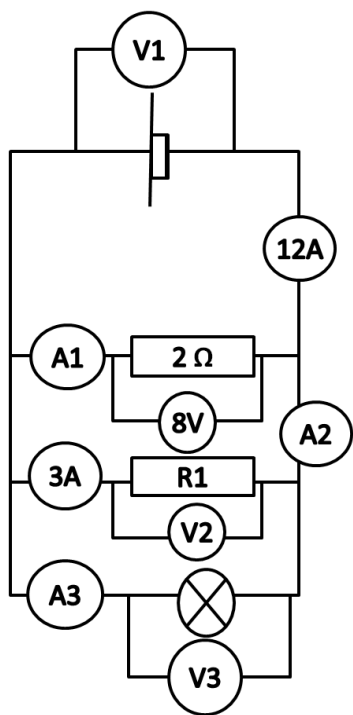1. Calculate the values at each point specified.



- A1 = _____
- A2 = _____
- A3 = _____
- V1 = _____
- V2 = _____
- V3 = _____
- R1 = _____

5. You have the power!

Keywords: power, Watt, current, potential difference, resistance

Objectives this tutorial:

- A) Calculating power using current and resistance
- B) Calculating power using Ohm's law
- C) Calculating energy from power

Starter:

What is the equation that links potential difference, current and power?



Objective A: Calculating power using current and resistance

There are two key equations that we have learnt so far.

Ohm's law states that:

Potential difference The amount of energy transferred by each Coulomb	=	Current The number of Coulombs that flow each second	X	Resistance How hard it is for charge to flow through a component
---	---	--	---	--

Power is related to current and potential difference using the equation:

Power The amount of energy transferred each second	=	Current The number of Coulombs that flow each second	X	Potential difference The amount of energy transferred by each Coulomb
--	---	--	---	---

There's one more equation to learn and we can work it out using these equations.

Practice A: Calculating power using current and resistance

1. What is potential difference in terms of current and resistance?
2. Substitute this into the equation for power (replace the 'V' in the power equation with your answer to question 1). You should have an equation that links power, current and resistance.
3. Use your equation to calculate the power in a circuit that has a current of 4 A and a resistance of 10 Ω

- A hairdryer has a power of 220 W and runs off a 5 amp current. Calculate the resistance of the hairdryer.
- A 900 W microwave has a resistance of 6 Ω . Calculate the current flowing through the microwave. Give your answer to three significant figures.

Assessment A: Calculate potential difference in series and parallel circuits

Which equation is incorrect?

A	$P = I^2R$
B	$R = V/I$
C	$V = I/P$
D	$I = \sqrt{(P/R)}$


Objective B: Calculating power using Ohm’s law

These two equations are often used in conjunction with one another. You might be asked to calculate power, but only be provided with resistance and potential difference.

All you have to do is use one equation, followed by the other equation.

It's easy to spot these questions in a physics exam because they are usually worth between 4 and 6 marks!

It's easy money.

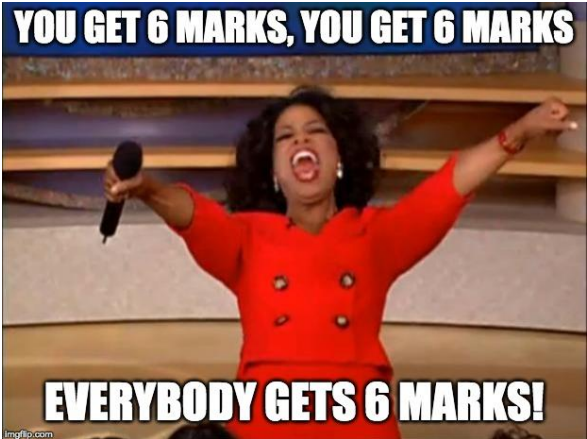

For a video on calculating current using ohms law click here: <https://www.youtube.com/watch?v=VX1P957sbGU>

Worked example

The heating element of a 2.3 kW electric kettle takes a current from a 230 V mains electricity supply. Calculate the resistance of the heating element.

Step 1 – write down what you know and what you want to know

Power = 2.3 kW
Potential difference = 230 V
Resistance = ?

Step 2 - what equation links the information that you know?

$P = IV$

Step 3 – Calculate the first unknown

$2.3 \text{ kW} = 2300 \text{ W}$ ← convert your units

$2300 \text{ W} = I \times 230 \text{ V}$ ← substitute in values

$I = 2300 \text{ W} / 230 \text{ V}$ ← rearrange

$I = 10 \text{ A}$ ← units

Step 4 – what equation can you now use to find your unknown?

$V = IR$
OR
 $P = I^2R$

Step 5 – calculate the unknown value

$V = IR$

$230 \text{ V} = 10 \times R$ ← substitute in values

$R = 230 \text{ V} / 10 \text{ A}$ ← rearrange

$R = 23 \Omega$ ← units

Practice B: Calculating power using Ohm's law

1. Calculate the resistance of a 12 V car headlamp of power 36 W

2. A heater has a resistance of 17Ω and is used on a 230 V mains supply. Find the power to two significant figures.

3. An iron is rated at 3.5 A, 750 W.
- a) What is the potential difference across the iron?
 - b) What would the power be if the current was increased to 4.5 A?
4. The battery powers 4 motors in the drone. Each motor has a resistance of $1.60\ \Omega$ when the power input to each motor is 19.6 W. The 4 motors are connected in parallel with the battery.
Calculate the current through the battery.
5. The charge that flows through lawnmower in 8.5 minutes is 16 320 C. It has a power of 18.3 kW. Calculate the resistance of the heating element in the new shower.
Give your answer to three significant figures.
Write down any equations you use.

Assessment B: Calculating power using Ohm's law

You are provided with charge, time and potential difference. Which equations would you use to calculate power?

A	$V = IR$ and $P = I^2R$
B	$I = Q/t$ and $P = I^2R$
C	$I = Q/t$ and $P = IV$
D	$I = Q/t$, $R = V/I$ and $P = I^2R$

Objective C: Calculating energy from power

One more equation to learn. We already know that power is the amount of energy transferred each second.

We can write this mathematically by saying:

$$\text{Power (W)} = \text{Energy transferred (J)} / \text{Time (s)}$$

OR

$$\underline{\underline{P = E/t}}$$

Worked example

An electric heater draws a current of 8 amps (A) when plugged into the 230 V mains electricity supply. How much energy is transferred in 20 minutes? Give your answer in KJ.

Step 1 – write down what you know and want to know

$$I = 8 \text{ A}$$

$$V = 230 \text{ V}$$

$$T = 20 \times 60 = 1200 \text{ s} \quad \leftarrow \text{convert your units}$$

$$E = ?$$

Step 2 - what equation links the information that you know?

$$P = IV$$

Step 3 – Calculate the first unknown

$$P = 8 \text{ A} \times 230 \text{ V} \quad \leftarrow \text{substitute in values}$$

$$P = 1840 \text{ W} \quad \leftarrow \text{units}$$

Step 4 – what equation can you now use to find your unknown?

$$P = E/t$$

Step 5 – calculate the unknown value

$$1840 \text{ W} = E/1200 \text{ s}$$

$$E = 1840 \text{ W} \times 1200 \text{ s} \quad \leftarrow \text{rearrange}$$

$$E = 2,208,000 \text{ J}$$

$$E = 2208 \text{ KJ} \quad \leftarrow \text{units}$$

Practice C: Calculating energy from power

1. Calculate the energy transferred by a 1.5 W torch over its lifetime of 30 hours
2. A 6 V battery passes a current of 0.3 A through a torch bulb for 5 minutes. How much energy is transferred from the cell? Give your answer in KJ.
3. An electric light bulb is labelled 100 W and is designed to be used with a p.d. of 230 V. What current flows in it, and how much energy is transferred in 1 hour?
4. The battery in the drone can store 97.5 kJ of energy.
When the drone is hovering, the power output of the battery is 65.0 W
Calculate the time for which the drone can hover.

5. (EXTRA MEATY) An immersion heater has a resistance of $17\ \Omega$ and is used on a 230 V mains supply.
 How long would it take to raise the temperature of 50 kg of water from $14\ ^\circ\text{C}$ to $58\ ^\circ\text{C}$?
 Assume that the specific heat capacity of water is $4200\ \text{J kg}^{-1}\ \text{K}^{-1}$.
 Energy (J) = mass (kg) x specific heat capacity x temperature change ($^\circ\text{C}$)

Assessment C: Calculating energy from power

Instead of Watts, what units should power actually be measured in?

A	J/s
B	Js
C	s/J
D	J/t

6. Final assessment



Reflecting on this booklet.

What did you most enjoy about Uni Pathways?
<ul style="list-style-type: none">•••

What did you find challenging about the programme?	How did you overcome these challenges?
<ul style="list-style-type: none">•••	<ul style="list-style-type: none">•••

Notes



Current events


Key Stage 4 Programme

researchersinschools.org



Lesson 1	Answers
A1	$I \frac{Q}{T}$
A2	It is the speed at which the charge is flowing. It is an amount of flow over time – in this case coulombs per second.
A3	It is negative because it is carried by delocalised electrons, which are negatively charged
A4	$\frac{18}{6} = 3$ 3A
A5	$3 \times 6.2 \times 10^{18} = 18.6 \times 10^{18}$
Assessment A	B
B1	$\frac{56,700}{2.5} = 22,680A$
B2	$8.5 \times 0.5 = 4.25$
B3	3×10^{-4}
B4	6kc = 6000c $250mA \div 1000 = 0.25A$ $6 \times 60^2 = 21600 \text{ seconds}$ $0.25A \times 21600 = 5400$ $5400 \div 6000 = 90\%$
B5	$5A = \frac{Q}{300}$ $= 1500C$
Assessment B	B
C1	1.2
C2	Tom
C3	$I_1 = I_2 + I_3$
C4	A4 = 0.07
Assessment C	D

Lesson 2	Answers
A1	The difference in how much energy each coulomb of charge has at two points in a circuit.
A2	$\frac{J}{C}$
A3	9v
A4	No energy is being transferred to the coulombs in the circuit
Assessment A	C
B1	6 V
B2	12v
B3	$V_1 = 6v$ $V_2 = 3v$ $V_3 = 3v$
B4	The bulb at V_1 will be the brightest because it has the most energy being transferred to it

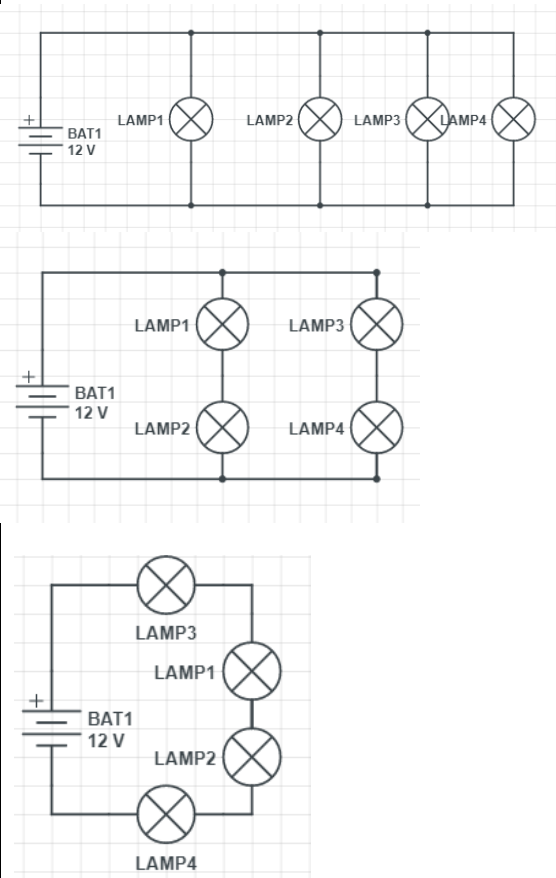Assessment B	
C1	$P = IV$
C2	57.5W
C3	0.5A
C4	230V
Assessment C	1495W

Lesson 3	
A1	Difficult for the charge to flow through
A2	A wooden pole would be more of an insulator
A3	47M Ω
A4	Current decreases
A5	Current halves
Assessment A	C
B1	Less than 1 OR >1
B2	25.3 Ω
B3	Decreases brightness
B4	R
B5	>6 and <10.5
Assessment B	A = 25 B = >6



C1	V=IR If resistance is constant and V and I are proportional
C2	Halves because they are directly proportional
C3	2.5 ohms
C4	A1 = 8A A2 = 5A A3 = 5A V1 = 20 V V2 = 20V V3 = 20V R1 = 6.67 Ohms
C5	A1 = 3A V1 = 9V V2 = 5V Bulb = 2.5 Ohms Resistor = 2 Ohms
Assessment C	A1 = 4A A2 = 8A A3 = 5A V1 = 8V V2 = 8V V3 = 8V R1 = 2.67 Ohms

Lesson 4	
A1	$V = IR$
A2	$P = IV$ $P = I(IR)$ $P = I^2R$
A3	160W
A4	8.8Ω
A5	12.2A
Assessment A	C
B1	4Ω
B2	1A
B3	964.3W
B4	7A
B5	17.9Ω
Assessment B	C
C1	45J
C2	0.009KJ
C3	360KJ
C4	25 mins
C5	~ 49.5 minutes give or take 30 seconds depending on rounding




Assessment C	A

Q1.

Figure 1 shows the circuit symbol for three different components.

Figure 1

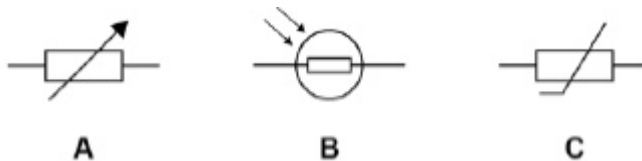

(a) Which component is a variable resistor?

Tick **one** box.

A ☐

 B ☐

 C ☐

(1)

(b) In which component will the resistance decrease when the temperature increases?

Tick **one** box.

A ☐


 B ☐

 C ☐

(1)

Figure 2 shows four different arrangements of resistors.

Figure 2

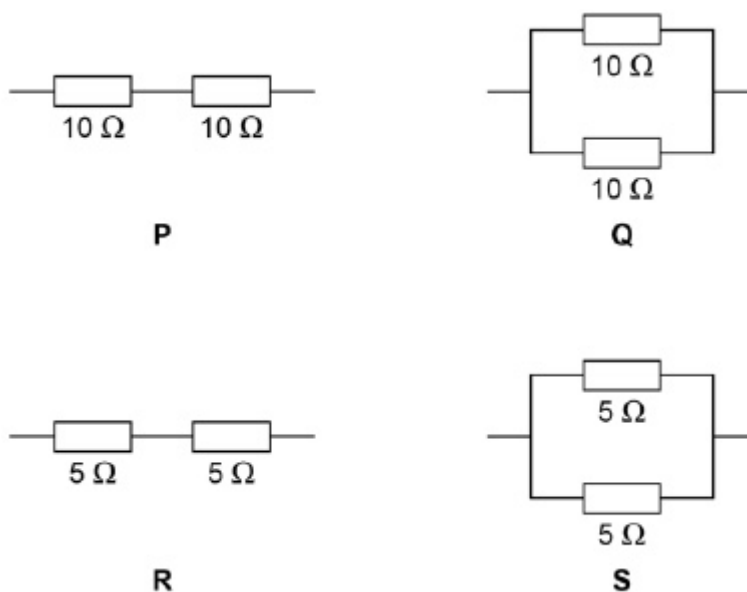

- (c) Two of the arrangements are in series and two are in parallel.

Describe the difference between a series and a parallel arrangement.

(2)

- (d) Which arrangement has a resistance of $10\ \Omega$?

Tick **one** box.

P ☐ Q ☐ R ☐ S ☐

(1)

- (e) Which arrangement has the highest resistance?

Tick **one** box.

P ☐ Q ☐ R ☐ S ☐

(1)

- (f) A student connects a resistor to a cell for 60 seconds.

The current through the resistor is $0.97\ \text{A}$

Calculate the charge flow.

Use the equation:

$$\text{charge flow} = \text{current} \times \text{time}$$

Give your answer to 2 significant figures.

Charge flow = _____ C

(3)


(Total 9 marks)

Q2.

Figure 1 shows a circuit diagram containing two identical lamps arranged in parallel.

The reading on the ammeter is 186 mA.

Figure 1

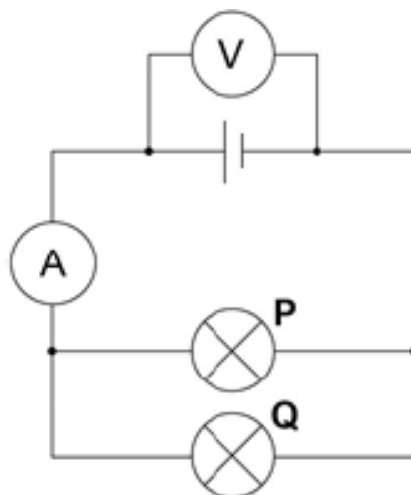

- (a) Which statement about the current through the lamps is true?

Tick **one** box.

The current through both lamp **P** and lamp **Q** is
0.093 A

☐

The current through both lamp **P** and lamp **Q** is
0.186 A

☐

The current through both lamp **P** and lamp **Q** is
0.93 A

☐


The current through both lamp **P** and lamp **Q** is
1.86 A

☐

(1)

- (b) **Figure 2** shows a circuit that can be used to alter the brightness of a lamp.

Figure 2

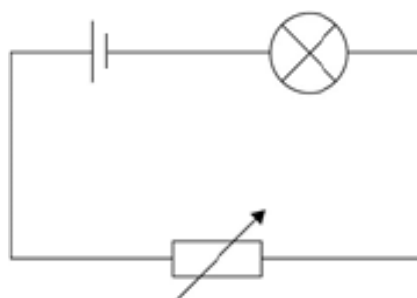

The resistance of the variable resistor is increased.

What effect will this have on the brightness of the lamp?

Explain your answer.

(2)

- (c) When the potential difference across the lamp is 3.3 V, the current is 0.15 A.

Write down the equation that links current, potential difference and resistance.

Equation _____

(1)

- (d) Calculate the resistance of the lamp.

Resistance = _____ Ω

(3)


(Total 7 marks)

Q3.

A student built a circuit using filament lamps.

- (a) Sketch a current potential difference graph for a filament lamp on **Figure 1**


Figure 1

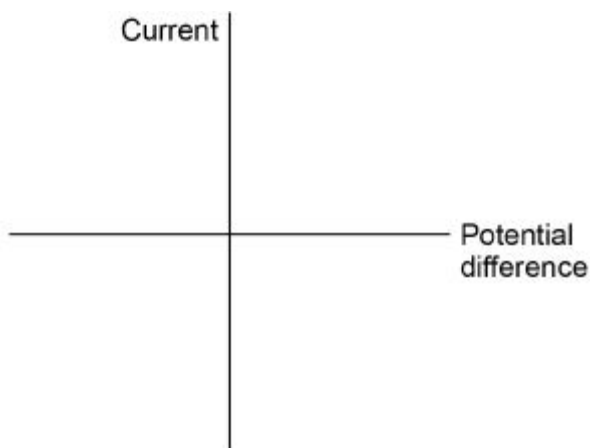

(2)

Figure 2 shows the circuit with two identical filament lamps.

Figure 2

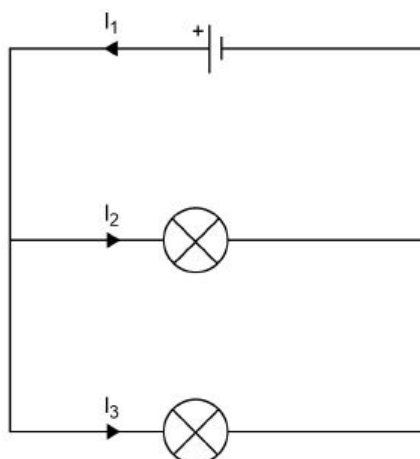

- (b) Compare the currents I_1 , I_2 and I_3

(2)

- (c) Calculate the charge that flows through the cell in 1 minute. Each filament lamp has a power of 3 W and a resistance of $12\ \Omega$

Write any equations that you use.

Give the unit.

Charge = _____

Unit = _____

(6)

(Total 10 marks)

Q4.

The current in a circuit depends on the potential difference (p.d.) provided by the cells and the total resistance of the circuit.

- (a) Using the correct circuit symbols, draw a diagram to show how you would connect 1.5 V cells together to give a p.d. of 6 V.


(2)

- (b) **Figure 1** shows a circuit containing an 18 V battery.

Two resistors, **X** and **Y**, are connected in series.

- **X** has a resistance of $3\ \Omega$.
- There is a current of 2 A in **X**.

Figure 1

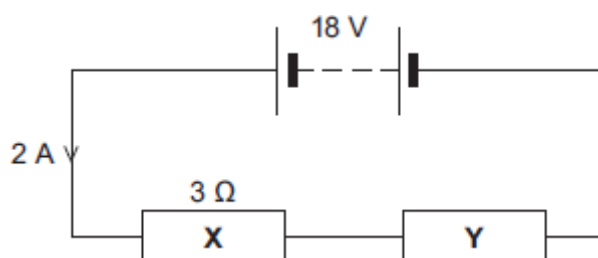

- (i) Calculate the p.d. across **X**.

P.d. across **X** = _____ V

(2)

- (ii) Calculate the p.d. across **Y**.

P.d. across **Y** = _____ V

(2)

- (iii) Calculate the total resistance of **X** and **Y**.

Total resistance of **X** and **Y** = _____ Ω

(2)

(Total 8 marks)

Mark schemes

Q1.

- | | | |
|-----|---|---|
| (a) | A | 1 |
| (b) | C | 1 |
| (c) | a series circuit has only one path/loop/branch | 1 |
| | a parallel circuit has a branch(es) to provide more than one path / loop | |
| | <i>allow answers that describe the difference in terms of potential difference, current or resistance</i> | 1 |
| (d) | R | 1 |
| (e) | P | 1 |
| (f) | $Q = 0.97 \times 60$ | 1 |
| | $Q = 58.2$ (C) | 1 |
| | $Q = 58$ (C) | |
| | <i>an answer of 58 (C) scores 3 marks</i> | 1 |
- [9]**

Q2.

- | | | |
|-----|---|---|
| (a) | 0.093 A | 1 |
| (b) | (increasing the resistance) decreases the current | 1 |
| | therefore (the lamp will be) dimmer | 1 |
| (c) | potential difference = current \times resistance | |
| | <i>accept correct rearrangement with R as subject</i> | 1 |
| (d) | $3.3 = 0.15 \times R$ | 1 |
| | $R = 3.3 / 0.15$ (Ω) | 1 |
| | $R = 22$ (Ω) | 1 |

Q3.

- (a) a curve in the first and third quadrants only, passing through origin

1

decreasing gradient

1

- (b) any **two** from:

- $I_1 = I_2 + I_3$
- $I_2 = I_3$
- $I_1 = 2I_2$
- $I_1 = 2I_3$

allow 1 mark for each correct description given in words

2

- (c) $3 = I^2 \times 12$

1

$$I = \sqrt{\left(\frac{3}{12}\right)}$$

1

$$I = 0.5 \text{ (A)}$$

1

$$Q = 0.5 \times 60 = 30$$

allow $Q =$
their calculated $I \times 60$

1

$$Q_{\text{total}} = 60$$

allow an answer that is consistent with their
calculated value of I

1

or

$$3 = I^2 \times 12 \text{ (1)}$$

$$I = \sqrt{\left(\frac{3}{12}\right)}$$

$$I = 0.5 \text{ (A) (1)}$$

$$I_{\text{total}} = 1.0 \text{ (A) (1)}$$

allow $I_{\text{total}} = \text{their } I \times 2$

$$Q = 1.0 \times 60 = 60 \text{ (1)}$$

allow an answer that is consistent with their

calculated value of I

coulombs **or** C

1

an answer of 60 scores 5 calculation marks

[10]

Q4.

- (a) *attempt to draw four cells in series*

1

correct circuit symbols

*circuit symbol should show a long line and a short line,
correctly joined together*

example of correct circuit symbol:



1

- (b) (i) 6 (V)

allow 1 mark for correct substitution, ie

$V = 3 \times 2$ scores 1 mark

provided no subsequent step

2

- (ii) 12 (V)

ecf from part (b)(i)

$18 - 6$

or

$18 -$ their part (b)(i) scores 1 mark

2

- (iii) 9 (Ω)

ecf from part (b)(ii) correctly calculated

$3 +$ their part (b)(ii) / 2

or

$18 / 2$ scores 1 mark

provided no subsequent step

2

[8]

Q1.

- (a) Complete the sentence.

Choose the answer from the box.


charge	energy	potential difference	resistance
--------	--------	----------------------	------------

Electric current is the rate of flow of _____.

(1)

Figure 1 shows a parallel circuit.

Figure 1

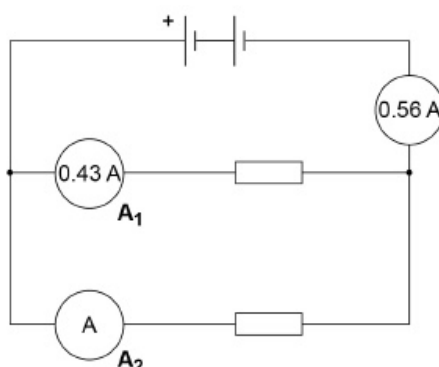

- (b) Calculate the current measured by ammeter **A₂**.

Current = _____ A

(1)

- (c) The circuit is connected for 300 s

The total current in the circuit stays at 0.56 A

Calculate the total charge flow.

Use the equation:

$$\text{charge flow} = \text{current} \times \text{time}$$

Charge flow = _____ C

(2)

- (d) The potential difference supplied by the battery is 4.5 V

Calculate the total energy transferred in 300 s

Use the equation:

$$\text{energy transferred} = \text{charge flow} \times \text{potential difference}$$


Use your answer to part (d).

Energy transferred = _____ J

(2)

- (e) **Figure 2** shows a series circuit.

Figure 2

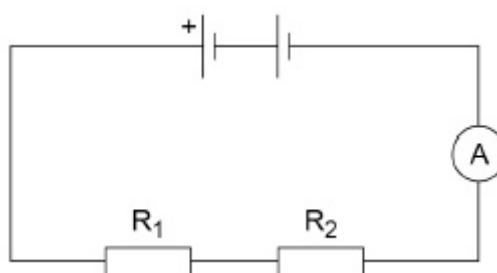


Resistor **R₂** breaks.

What happens to the reading on the ammeter?

(1)

- (f) **Figure 3** shows a parallel circuit.

Figure 3

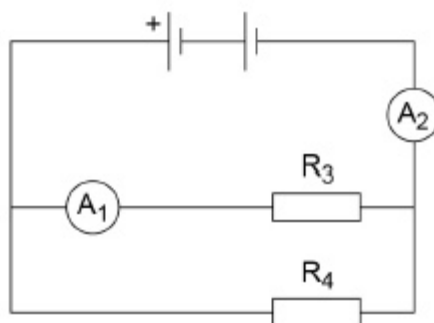

Resistor R_3 breaks.

What happens to the readings on the ammeter?

Ammeter A_1 _____


Ammeter A_2 _____

(2)

Q2.

A student investigates how the length of a piece of wire affects its resistance.

The diagram shows the apparatus used.

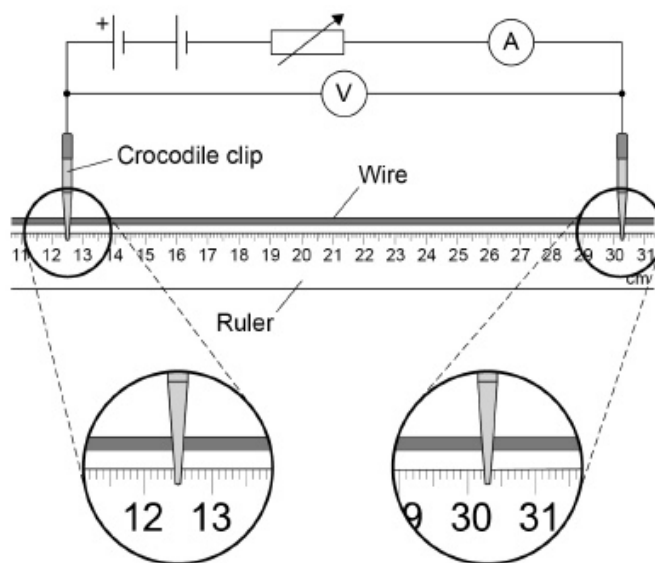

- (a) Write the equation which links current, potential difference and resistance.

(1)

- (b) For the experiment shown in the diagram, the student recorded:
- a potential difference of 3.22 V
 - a current of 2.18 A

Calculate the resistance of the length of wire between the crocodile clips.

Give your answer to 3 significant figures.

Resistance = _____ Ω (4)

- (c) The student used constantan wire.


The resistance of constantan only changes a small amount when its temperature changes.

Suggest why using constantan is an advantage in this experiment.

(2)

Q3.

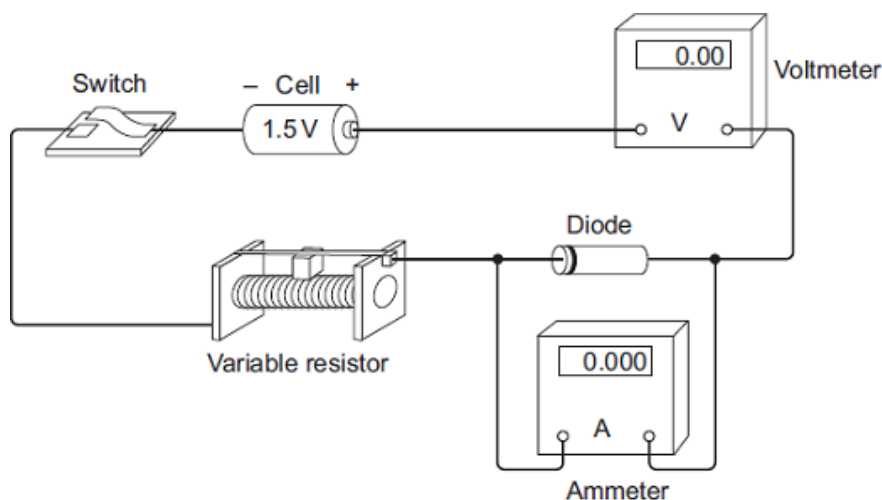- (a) A student set up the circuit shown in the diagram. The student uses the circuit to obtain the data needed to plot a current - potential difference graph for a diode.



- (i) Draw, in the boxes, the circuit symbol for a diode and the circuit symbol for a variable resistor.

Diode

Variable resistor

(2)


- (ii) The student made two mistakes when setting up the circuit.

What **two** mistakes did the student make?

1. _____

2. _____

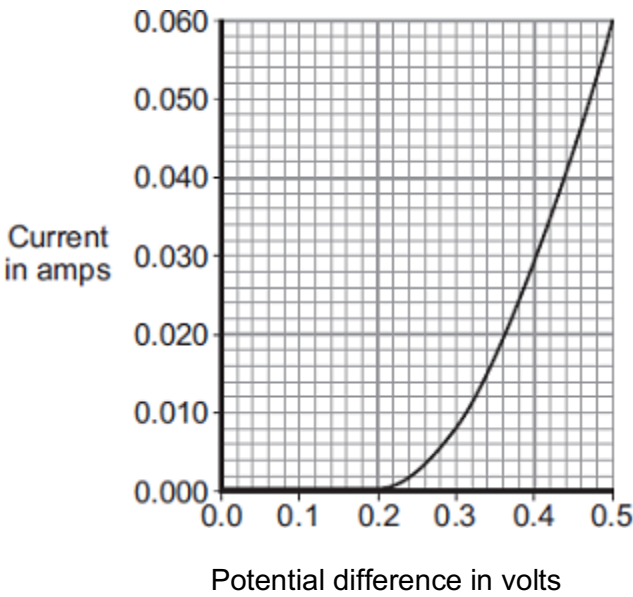- (b) After correcting the circuit, the student obtained a set of data and plotted the graph below.



- (i) At what potential difference did the diode start to conduct an electric current?

_____ V

(1)


- (ii) Use data from the graph to calculate the resistance of the diode when the potential difference across the diode is 0.3 V.

Resistance = _____ ohms

(3)

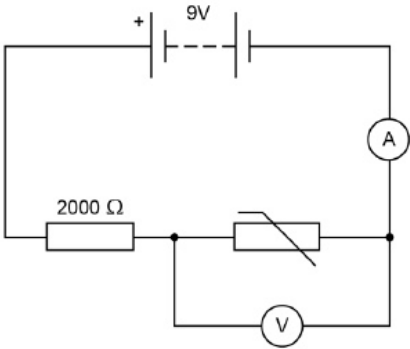Q4.

The diagram shows a temperature sensing circuit used to control a heating system



- (a) What quantity does the ammeter measure?

(1)

- (b) The current in the circuit is 3.5 mA when the potential difference across the thermistor is 4.2 V

Calculate the resistance of the thermistor.

Resistance = _____ Ω

(3)

- (c) Calculate the charge that flows through the thermistor in 5 minutes when the current is 3.5 mA.

Charge = _____ C

(3)

- (c) The charge that flows through a new shower in 300 seconds is 18 000 C.
The new electric shower has a power of 13.8 kW.

Calculate the resistance of the heating element in the new shower.

Write down any equations you use.


Resistance = _____ Ω

(5)

Mark schemes

Q1.

(a)

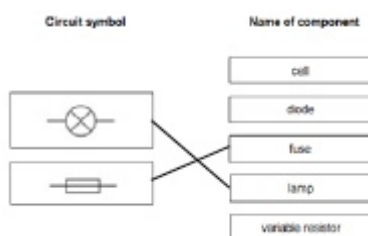

extra lines from circuit symbols negate the mark

1
1

(b) charge

1

(c) 0.13 (A)

1

(d) 0.56×300

1

168 (C)

an answer of 168 (C) scores 2 marks

1

(e) 168×4.5

1

756 (J)

*an answer of 756 (J) scores 2 marks
allow ecf from part (d)*

1

(f) decreases to zero

allow reads zero

1

(g) (A1) decreases to zero

allow reads zero

1

(A2) decreases

*do **not** accept 'to zero' for A2*

1

(h) thermistor

1

(i) answer in range 160–165 (Ω)

Q2.

- (a) 17.8

accept 17.7 or 17.9

1

- (b) potential difference = current \times resistance

accept $V = IR$

1

- (c) $3.22 = 2.18 \times R$

1

$$R = 3.22/2.18$$

1

$$R = 1.477(064...) \Omega$$

1

$$R = 1.48 (\Omega)$$

an answer of 1.48 (Ω) scores 4 marks

an answer that rounds to 1.48 (Ω) scores 3 marks

1

- (d) temperature of wire will increase during experiment

allow description of this in terms of energy being dissipated,

$$P = I^2 R$$

1

if constantan is used, this will not have a significant effect on results

1

- (e) 50.0 cm

allow other ways of indicating the anomalous result in the table (eg ringing 5.26)

1

- (f) the ammeter gave a reading that was too low

1

[10]

Q3.

- (a) (i) 1.7

1

- (ii) 51

or

30 \times their (i) correctly calculated

$$= \frac{Q}{30}$$

allow 1 mark for correct substitution i.e. 1.7

$$= \frac{Q}{30}$$

or their (i)

coulomb / C
do **not** accept c

1

- (iii) 612
or
their (ii) $\times 12$ correctly calculated
or
their (i) $\times 360$ correctly calculated
allow **1** mark for correct substitution i.e. $E = 12 \times 51$
or $12 \times$ their (ii)
or their (i) $\times 360$

2

- (b) ions vibrate faster
or
ions vibrate with a bigger amplitude
accept atoms for ions throughout
accept ions gain energy
accept ions vibrate more
ions start to vibrate is insufficient

1

electrons collide more (frequently) with the ions
or
(drift) velocity of electrons decreases
electrons start to collide is insufficient
there are more collisions is insufficient, unless both electrons
and ions are implied

1

[8]


Q4.

- (a) (i) symbol for a diode



1

symbol for a variable resistor

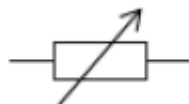

1

- (ii) voltmeter is in series or voltmeter is not in parallel

1

ammeter is in parallel or ammeter is not in series
accept an answer in terms of how the circuit should be
corrected
voltmeter and ammeter are wrong way around is insufficient

- (b) (i) 0.2 (V)
accept any value between 0.20 and 0.21 inclusive
1
- (ii) 37.5
allow 1 mark for $I = 0.008$
or
allow 2 marks for correct substitution, ie $0.3 = 0.008 \times R$
or
allow 1 mark for a correct substitution using $I = 0.8$ or $I = 0.08$
or $I = 0.009$
or
allow 2 marks for answers of 0.375 or 3.75 or 33(.3)
3
- (c) (i) 25
allow 1 mark for obtaining period = 0.04(s)
2
- (ii) diode has large resistance in reverse / one direction
1
- so stops current flow in that / one direction
allow diodes only let current flow one way / direction
allow 1 mark for the diode has half-rectified the (a.c. power) supply
1
- [12]

Q1.

- (a) current
1
- (b) $4.2 = 3.5 \times 10^{-3} \times R$
1
- $R = 4.2 / 3.5 \times 10^{-3}$
1
- $R = 1200 (\Omega)$
an answer of 1200 (Ω) scores 3 marks
an answer of 1.2 scores 2 marks
1
- (c) conversion from minutes to seconds (300 s)
1
- $Q = 0.0035 \times (5 \times 60)$
1
- $Q = 1.05 \text{ C}$
an answer of 1.05 (C) scores 3 marks

an answer of 17.5 scores **1** mark
 an answer of 1050 or 0.0175 scores **2** marks

1


(d) (potential difference) increases

1

(because thermistor) resistance increases

2nd mark dependent on scoring 1st mark

1

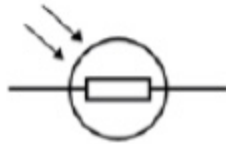

(e)

1

[10]

(c) $18000 = I \times 300$

1

$$I = 18000 / 300 = 60$$

1

$$13\,800 = (60^2) \times R$$

1

$$R = 13\,800 / 60^2$$

1

$$3.83 (\Omega)$$

1

allow 3.83(Ω) with no working shown for **5** marks

answer may also be correctly calculated using $P = IV$ and $V = IR$ if 230 V is used.